

## **Choice of Components and Design Justification**

### **Project Description:**

A 5 V, 3 A DC–DC buck converter was designed in **KiCad Software** using the LM2596S-5 IC, including schematic, PCB layout, and 3D verification to ensure stable performance and manufacturability

#### **1. Buck Regulator IC – LM2596S**

- The selection of the LM2596S-5 chip was based on its ability to regulate output at a constant 5 V with a maximum of 3 A current, satisfying the design specifications.
- This chip allows the voltage range required in the design to be realized without requiring external voltage dividers since it has the power switch incorporated inside.
- This eliminates errors on the design since it does not involve the use of feedback resistors as in the case of other designs that can be prone to errors.

#### **2. Inductor - 33μH Power Inductor**

- The value of the inductor is determined based on the required current ripple and the switching frequency to ensure that the system is stable.
- A standard inductor of 33 μH is selected based on the fact that its value is approximately equal to the calculated one, as well as its ability to aid in reducing current rips.
- The selected inductor is capable of handling the current above the peak current.

#### **3. Freewheeling Diode – SS54 Schottky**

- The SS54 Schottky diode is employed due to low forward voltage drop and quick switching times.
- This contributes to reduced power loss and higher efficiencies. It should be noted that the current and voltage handling capabilities of the diode exceed the specifications, ensuring an appropriate margin of safety during operation.

#### **4. Input Capacitors – 220 μF Electrolytic and 100 nF Ceramic**

- A 220μF electrolytic capacitor is used at the input end for smoothing the voltage and providing the current during the switching process.
- A 100 nF capacitor is connected in parallel to filter high-frequency noises.
- Both of these capacitors help in providing a stable and clean input voltage to the voltage regulator.

#### **5. Output Capacitors – 330 μF Low-ESR Electrolytic and 100nF Ceramic**

- A low ESR electrolytic capacitor of 330 μF is used at the output in order to stabilize the output voltage and ensure a ripple of less than 50 mV.
- The low ESR is of importance in the reduction of the ripple effect due to the changes in current. A 100 nF ceramic capacitor is used as a filter of high-frequency noise.

## **6. Protection and Indicator Components**

- A TVS diode is added at the input. This is used as a protection mechanism for the circuit from voltage spikes and ESD.
- An LED and a current-limiting resistor are connected at the output. The LED is used as an indication that the output is at the required 5V.
- These components improve safety and make it easier to check proper operation.

### **Final Conclusion:**

- A 5 V, 3 A buck converter was designed using the LM2596S-5 regulator to meet the specified input voltage range and load requirements. Component values were selected based on worst-case design calculations and validated against current, voltage, and ripple limits.
- The inductor, diode, and capacitors provide stable regulation, low output ripple, and sufficient operating margin under full load. Output ripple voltage remains within the specified 50 mV limit, ensuring reliable performance.
- The fixed-output architecture simplifies implementation while maintaining accurate and consistent voltage regulation.
- Overall, the design satisfies all functional, electrical, and reliability requirements.