

**MOHAMED SAHUL HAMEED H**

**4<sup>TH</sup> YEAR, B.E ECE,**

**CEG CAMPUS, ANNA UNIVERSITY**

## **DESIGN CALCULATIONS**

### **5 V DC–DC Buck Converter using LM2596S-5**

#### **Given Specifications:**

- Input Voltage  $V_{in} = 6\text{ V} - 20\text{ V}$
- Output Voltage  $V_{out} = 5\text{ V}$
- Load Current  $I_o = 3\text{ A}$
- Switching Frequency  $f_s = 150\text{ kHz}$
- Output Ripple Voltage  $< 50\text{ mV}$

#### **1.Duty Cycle Calculation:**

$$D = V_{out} / V_{in(max)}$$

$$D = 5 / 20$$

$$\mathbf{D = 0.25}$$

➤ **Note:**

Duty cycle tells how long the switch inside the IC is ON. We calculate it at maximum input voltage because that is the worst operating condition.

#### **2.Inductor Ripple Current:**

$$\Delta I_L = 0.3 \times I_o$$

$$\Delta I_L = 0.3 \times 3$$

$$\mathbf{\Delta I_L = 0.9\text{ A}}$$

➤ **Note:**

Ripple current is the small up-and-down change in inductor current. We choose about 30% of load current to keep the circuit stable and efficient

#### **3. Inductor Value Calculation:**

$$L = [ V_{out} \times (V_{in} - V_{out}) ] / [ V_{in} \times \Delta I_L \times f_s ]$$

$$\Delta I_L = 0.3 \times 3$$

$$L = [ 5 \times (20 - 5) ] / [ 20 \times 0.9 \times 150000 ] = \mathbf{L = 27.8\text{ }\mu\text{H}}$$

➤ **Note:**

Ripple current is the small up-and-down change in inductor current. We choose about 30% of load current to keep the circuit stable and efficient

$$L = 33 \mu\text{H}$$

- 27.8  $\mu\text{H}$  is not a standard value, so we select the next higher standard value (33  $\mu\text{H}$ ) to reduce ripple and improve performance

#### 4. Actual Inductor Ripple Current:

$$\Delta I_L(\text{actual}) = \frac{V_o(V_{in}-V_o)}{V_{in} \cdot f_s \cdot L}$$

$$\Delta I_L(\text{actual}) = \frac{5(20-5)}{20(150\text{k})(0.33\mu)}$$

$$\Delta I_L(\text{actual}) = 0.76\text{A}$$

➤ **Note:**

After choosing the standard inductor value, we re-calculate ripple current to confirm it is within safe limits.

#### 5. Peak Inductor Current:

$$I_{L(\text{peak})} = I_o + (\Delta I_L / 2)$$

$$I_{L(\text{peak})} = 3 + (0.76 / 2)$$

$$I_{L(\text{peak})} = 3.38 \text{ A}$$

➤ **Note:**

Peak current is the highest current flowing through the inductor. The inductor must handle this current without saturating

#### 6. Output Capacitor Ripple Voltage (Capacitive):

$$\Delta V_C = \Delta I_L / (8 \times f_s \times C)$$

$$\Delta V_C = 0.76 / (8 \times 150000 \times 330\mu)$$

$$\Delta V_C \approx 1.9 \text{ mV}$$

➤ **Note:**

This ripple comes from the charging and discharging of the output capacitor during switching

## 7. Output Capacitor ESR Ripple Voltage:

$$\Delta V_{ESR} = \Delta I_L \times ESR$$

$$\Delta V_{ESR} = 0.76 \times 0.05$$

$$\Delta V_{ESR} = 38 \text{ mV}$$

➤ **Note:**

ESR is the small internal resistance of the capacitor. It causes most of the output voltage ripple.

## 8. Total Output Ripple Voltage:

$$\Delta V_{out} = \Delta V_C + \Delta V_{ESR}$$

$$\Delta V_{out} = 1.9 + 38$$

$$\Delta V_{out} = 39.9 \text{ mV}$$

➤ **Note:**

Total ripple voltage is within the allowed limit of 50 mV, so the design is acceptable.

## 9. Diode Current Check:

$$I_D \approx I_o = 3 \text{ A}$$

➤ **Note:**

The diode must handle the full load current. A Schottky diode is used to reduce losses and increase efficiency

## Design validation:

- The design calculations were carried out for a 5 V, 3 A buck converter using the LM2596S-5 IC.
- The inductor value was calculated based on the selected ripple current and a standard 33  $\mu\text{H}$  inductor was chosen.
- Peak inductor current was calculated to ensure the inductor operates without saturation. Output ripple voltage was computed and found to be less than the specified limit of 50 mV.
- Since a fixed-output regulator was used, the output voltage is inherently regulated at 5 V.
- Thus, the calculated values confirm that the design meets all required electrical specifications.